

## **Current Transformers for Protection Relays**

March 25, 2019

This **White Paper** describes the technical characteristics of Class C current transformers when used in protection relay applications.

Authored by:
Michael Mosman
Principal
Vice President and Senior Electrical Engineer

For more information contact:

Morrison Hershfield 1500 S Edgewood Street | Baltimore, MD 21227

Phone: 410-525-0010

www.morrisonhershfield.com


## **Current Transformers for Protection Relays**

Current transformers for protection relays, as opposed to those use strictly for metering purposes, have an IEEE standard classification. There are two classifications, Class T CTs and Class C CTs. The 'T' stands for "tested" and the 'C' stands for "computed".

Class T CTs generally have a high level of flux leakage (due to the way the primary is configured as multiple windings around the core) which requires the performance of the CT to be tested. Class T CTs are rarely used for commercial power system protection relays, and they will not be discussed further here.

Class C CTs have negligible flux leakage because the primary passes only once through the core "window" and the secondary is wound around the entire length of the core. The performance of Class C CTs can be derived (computed) from the manufacturer's published data for the CT. Nearly all CTs used for power protection are Class C.

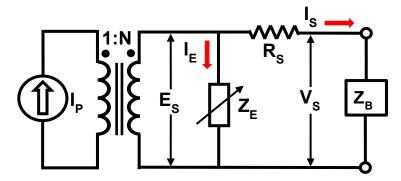A CT is merely a transformer that is current excited instead of voltage excited. Figure 1 shows an equivalent circuit for a current transformer. It includes an ideal transformer in which the primary is a single-turn winding connected to a current source.



N = Turns Ratio (pri. amps divided by sec. amps)

I<sub>p</sub> = Primary Amps (represented as current source)

I<sub>s</sub> = Secondary Amps (typically 1A or 5A)

I<sub>F</sub> = Excitation Amps (magnetizing current)

 $E_s$  = Secondary EMF (excitation volts)

V<sub>s</sub> = Secondary Terminal Volts

R<sub>s</sub> = Secondary Resistance (in ohms)

**Z**<sub>E</sub> = Excitation Impedance (in ohms, non-linear)

Figure 1 - CT Equivalent Circuit

The primary current I<sub>P</sub> induces flux in the core of the CT which produces an electromotive force (EMF), or voltage E<sub>S</sub>, in the secondary. The excitation impedance Z<sub>E</sub> represents an amalgamation of leakage reactance, eddy current resistance and flux hysteresis losses that acts as a shunt impedance, diverting some current across the ideal transformer secondary. This current (IE) is called the excitation current, or magnetizing current, and is non-linear. Because Z<sub>E</sub> has resistive and reactive components, so does I<sub>E</sub>. However, for simplicity I<sub>E</sub> is usually considered as an absolute value in ohms, and assumed to be in phase with the secondary terminal current Is.



## Technical White Paper | Current Transformers for Protection Relays

The impedance of the wires and relays that are connected to the CT is call the "burden," and is represented in the equivalent circuit as  $Z_B$ . This impedance is mostly resistive, so the small reactive component in  $Z_B$  is usually ignored.

The relationship between  $E_S$  and  $I_E$  is found in Excitation Curves provided by the manufacturer of the CT. The manufacturer also provides the secondary resistance  $R_S$  for the CT. These data usually appear as a chart showing excitation curves for a family of CTs with different ratios but all with the same C rating. A typical chart of excitation curves is shown in Figure 2.

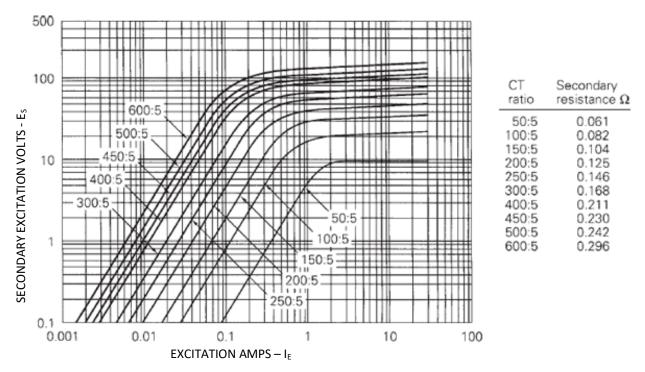


Figure 1 – Typical Excitation Curve Chart

The Engineer must make an assessment of the burden resistance in the protection design and choose a CT with performance ratings suitable to support the burden under normal and fault conditions. In general, this amounts to selecting the proper "C" rating.

The "C" Class rating of a protection CT is usually shown next to the CT ratio on drawings and performance charts, and is a value in volts. For example, a CT labeled "600:5 C100" has a ratio N = 30 (600/5) and a "C" rating of 100 volts. This voltage is a measure of the CT's performance under a fault condition. It represents the secondary voltage  $V_S$  that the CT is capable of producing while the primary circuit  $I_P$  is under fault and the secondary current  $I_S$  is 20 times the CT's secondary amps rating. Furthermore, while in this fault condition the "ratio error" of the CT will not exceed 10%. IEEE Standard 37.110 defines the ratio error of a Class C current transformer as  $I_E/I_S$ . That means for a CT having a 5A rated secondary, with  $I_S$  at 20 x 5A = 100A,  $I_E$  will not exceed 100A x 0.1 = 10A.

The ratio error of a CT is basically a measure of the accuracy of the CT. I<sub>E</sub> in a CT is current generated within the CT by the primary current that is "lost" and does not produce secondary terminal output current. This manifests itself as a slight difference between the CT's labeled ratio



## Technical White Paper | Current Transformers for Protection Relays

N and the actual ratio  $I_P:I_S$ . The result is that  $I_P$  will always be higher than N x  $I_S$  by the percentage of ratio error.

The accuracy (ratio error) of a Class C CT can be calculated using the information in the manufacturer's Excitation Curve Chart. For any value of  $I_S$  the excitation voltage  $E_S$  can be found if the burden  $Z_B$  is known:

$$E_S = I_S x (R_S + Z_B)$$

From the chart the value of IE can be derived, and from that the error ratio can be calculated. Notice that when  $Z_B$  becomes large, so does  $E_S$  and, consequently, so does  $I_E$  and the ratio error. The minimum "C" rating for a specific protection system CT must be able to support is dependent on the burden  $Z_B$ . By definition, the CT under fault must be able to sustain the "C" voltage rating with 100 amps flowing in the secondary terminals. Therefore, the voltage  $V_S$  = 100A x  $Z_B\Omega$ . In the example above, the 600:5 C100 CT would be appropriate for any burden up to 1 ohm (100A x  $I\Omega$  = 100V).

It is advisable to check the ratio error with the excitation chart for the CT. The value of ES can be found by adding the voltage drop across the secondary resistance  $R_{\rm S}$  to the secondary voltage  $V_{\rm S}$ . In the example, the 600:5 CT has a stated  $R_{\rm S}$  = 0.296 $\Omega$ . At 100A the voltage drop is 29.6V and  $E_{\rm S}$  is 100 + 29.6 = 229.6V. On the excitation curve for the 600:5 CT, this value of  $E_{\rm S}$  produces an excitation current  $I_{\rm E}$  is approximately 5 amps. This CT exhibits a ratio error of 5A / 100A + 5%. A ratio error of only 5% indicates this CT is conservatively rated, and a good choice for a relay and leads with 1 ohm burden.

Suppose it was given that a 600:5 C100 CT was already in place, and the maximum burden needed to be determined. The maximum ratio error of 10% prescribes an  $I_E$  of 10 amps which corresponds to an  $E_S$  of approximately 150 volts. Reducing that by the voltage drop through the 0.296 $\Omega$  R<sub>S</sub> experiencing 100A of  $I_S$  indicates that a V<sub>S</sub> of approximately 120 volts may still be with ratio accuracy limits. The CT has an effective "C" rating of 120, and would actually work acceptably with a burden up to 1.2 ohms. However, since "C" classifications come in standard voltages (20, 50, 100, 200, 400, 800) they can only be labeled with the highest standard "C" rating that falls below the actual CT capabilities.

Notice that this example has the maximum fault condition occurring above the knee of the excitation curve. This is typical. In fact, high-impedance differential relays (those with internal resistors that purposely raise the burden) are design to trip only when CTs operate in the saturated state, which is why those CTs usually have higher "C" ratings.

One final note: Current transformers with 1A secondary windings have only a  $20 \times 1A = 20A$  fault  $I_S$  and, therefore, require "C" ratings far below those for 5A CTs. For that reason alone 1A CTs should be seriously considered for complex protection systems.

